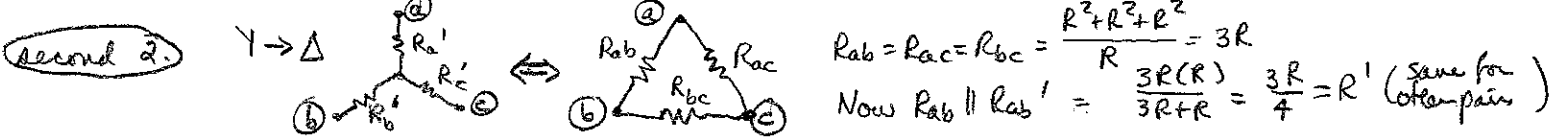


① a.  $V_3 = \frac{R_3}{(R_1+R_2)+R_3} V_s$  (V ÷)      b. let  $R_{eq} = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$ ;  $I_3 = \frac{R_{eq}}{R_{eq} + R_3} I_s$  (I ÷)

② a.  $R_2$  irrelevant since it is shorted.  $\Rightarrow \sum i = \frac{V_L - 0}{R_1} - I_s + \frac{V_L - 0}{R_L} = 0 \Rightarrow I_s = \frac{1}{10^3} + \frac{1}{10^3} = 2 \text{ mA}$

b. Power delivered to circuit  $P_{delivered} = V_L I_s = 2 \text{ mW}$






$R_{eq} = \frac{R'(2R')}{R'+2R'} = \frac{2(R')^2}{3R'} = \frac{2}{3} R' = \frac{2}{3} \left( \frac{3R}{4} \right) = \frac{R}{2} = R_{eq}$

3. Maximize power to load resistor  $R_L = 7 \parallel 3.08 = 2.12 \Omega$

$V_T$ :  $\sum_{abd} V = 0 = 440 - V_\Delta - 3(i_1 - i_2) - 220 \Rightarrow 3i_1 - 3i_2 + V_\Delta = 220$   
 $i_2 = 0.5i_1$      $V_\Delta = 2i_1 \Rightarrow i_2 = 0.5(2i_1) = i_1 \Rightarrow V_\Delta = 220$

so  $V_{oc} = V_T = V_\Delta + i_2 R = V_\Delta + i_1 R = V_\Delta + R \frac{V_\Delta}{2} = 220 \left( 1 + \frac{R}{2} \right)$

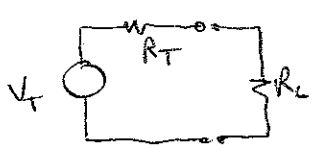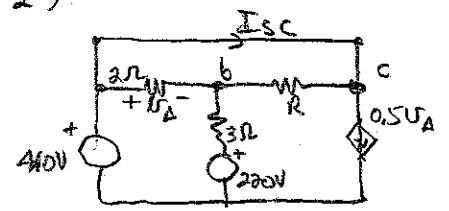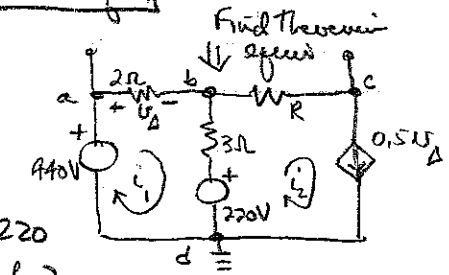$I_{sc}$ :  $\sum_i i = \frac{V_\Delta}{2} - \frac{(440 - V_\Delta) - 220}{3} - \frac{(440 - V_\Delta) - 440}{R} = 0 \Rightarrow V_\Delta = \frac{440R}{5R+6}$   
 $\sum_c i = I_{sc} - 0.5i_2 + \frac{(440 - V_\Delta) - 440}{R} = 0 \Rightarrow I_{sc} = \frac{R+2}{5R+6} (220)$



$V_T = 220 \left( 1 + \frac{R}{2} \right)$   
 $R_T = \frac{V_T}{I_{sc}} = \frac{[(R+2)/2] 220}{[(R+2)/(5R+6)] 220} = \frac{5R+6}{2}$   
 $R_L = 2.12 \Omega$

Max power @  $R_T = R_L \Rightarrow \frac{5R+6}{2} = 2.12 \Rightarrow 5R+6 = 4.24 - 6 \Rightarrow R < 0$   
not possible, so set  $R=0$  for max power transfer.