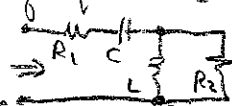


1.92 Find V_{RMS} for $w = V_m \sin \frac{2\pi}{T}t$ $0 \leq t \leq T/2$ $V_{RMS}^2 = \frac{1}{T} \left[\int_0^{T/2} V_m^2 \sin^2 \frac{2\pi}{T}t dt + \int_{T/2}^T 0 dt \right]$
 $V_{RMS}^2 = \frac{V_m^2}{2T} \int_0^{T/2} (1 - \cos \frac{4\pi}{T}t) dt = \frac{V_m^2}{2T} \left[\int_0^{T/2} dt - \int_0^{T/2} \cos \frac{4\pi}{T}t dt \right] = \frac{V_m^2}{4} \Rightarrow V_{RMS} = \frac{V_m}{2}$

2. 9.32 a. Freq of source adjusted to give i_g in phase w/ v_g . Find ω .
 Want $Z(s) \Rightarrow$  $Z(s) = R_1 + \frac{1}{sC} + \frac{sLR_2}{sL+R_2} = \frac{sR_1C+1}{sC} + \frac{sLR_2}{sL+R_2}$
 to be purely real: $= \frac{s^2(R_1+R_2)LC + s(L+R_1R_2C) + R_2}{sC(sL+R_2)}$


let $s \rightarrow j\omega \Rightarrow Z(j\omega) = \frac{a_1(R_2 - \omega^2(R_1+R_2)LC) + j\omega(L+R_1R_2C)}{-\omega^2LC + j\omega R_2C}$ $\frac{a_2(-\omega^2LC + j\omega R_2C)}{-\omega^2LC - j\omega R_2C}$ makes denominator purely real.

Numerator in the form $(a_1 + jb_1)(a_2 + jb_2)$; want that to be purely real as well $\Rightarrow j(a_1b_2 + a_2b_1) = 0$ or $(R_2 - \omega^2(R_1+R_2)LC)(\omega R_2C) + (-\omega^2LC)(\omega(L+R_1R_2C)) = 0$
 plug in numbers & obtain quadratic eq; solve to find $\omega = 2000 \text{ rad/s}$


b. If $v_g = 20 \cos 2000t \text{ V}$, find $v_o \rightarrow Z(j2000) = 500 - j500 + j(1000 \parallel 1000) = 1000 \Omega$
 $i_g = 20 \cos 2000t \text{ mA} \Rightarrow I_g = 20 \angle 0 \text{ mA}, V_g = 20 \angle 0 \text{ V}$
 $v_o = 10\sqrt{2} \cos(2000t + \pi/4) \text{ mA}$ \Rightarrow voltage $\Rightarrow v_o = \frac{(1000 \parallel 1000)}{500 - j500 + j(1000 \parallel 1000)} V_g = 10\sqrt{2} \angle \pi/4$

3. 9.40 $I_a = 2 \angle 0 \Rightarrow v_a = (50 + j150)(2 \angle 0) = 100 + j300 = 316 \angle 1.125 \text{ rad}$

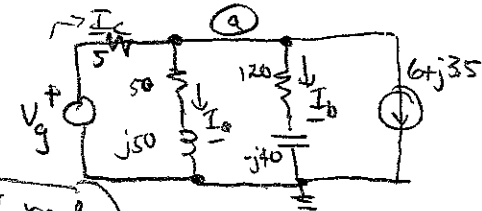a. Find I_b, I_c, V_g
 $I_b = \frac{316 \angle 1.125 \text{ rad}}{120 - j40} = 2.5 \angle \pi/2$
 $I_c = I_a + I_b + I_s = 2 + j2.5 + 6 + j3.5 = 8 + j6 = 10 \angle 0.64 \text{ rad}$
 $V_g = 5I_c + v_a = 5(8 + j6) + 100 + j300 = 140 + j330 = 358 \angle 1.17 \text{ rad}$



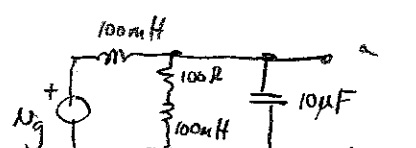
b. $\omega = 800 \text{ rad/s} \Rightarrow v_b(t) = 2.5 \cos(800t + \pi/2) \text{ A}$
 $i_c(t) = 10 \cos(800t + 0.64) \text{ A}$
 $v_g(t) = 358 \cos(800t + 1.17) \text{ V}$



$Z_L = j\omega L = j100 \Omega$
 $Z_C = -j/\omega C = -j100 \Omega$
 $Z_{RL} = 100 + j100 \Omega$


4. 9.41 $v_g = 247.49 \cos(1000t + \pi/4) \text{ V}$
 a. Find $V_T = \frac{Z_C \parallel Z_{RL}}{Z_L + Z_C \parallel Z_{RL}} V_g = \frac{(j100)(100 + j100)}{j100 + \frac{(j100)(100 + j100)}{100}} (247.49) \angle \pi/4 = 350 \angle 0^\circ$

b. Find Z_T (remove sources & look in) $\Rightarrow Z_T = Z_L \parallel Z_{RL} \parallel Z_C$ or $Y_T = \frac{1}{Z_T} = \frac{1}{Z_L} + \frac{1}{Z_{RL}} + \frac{1}{Z_C}$
 $Y_T = \frac{1}{j100} + \frac{1}{100 + j100} + \frac{1}{-j100} = \frac{1}{100\sqrt{2}} \angle \pi/4 \Rightarrow Z_T = 100\sqrt{2} \angle \pi/4 = 100 + j100$





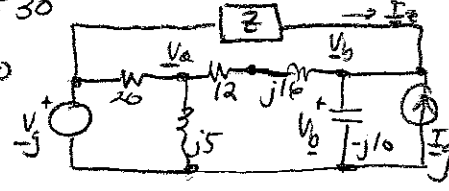
5. 9.63 Find Z if $v_g = 100 - j50$, $I_g = 30 + j20$, $v_b = 140 + j30$

$\sum I = \frac{v_g - v_a}{20} - \frac{v_a}{j5} - \frac{v_a - v_b}{12 + j16} = 0 \Rightarrow \frac{100 - j50 - v_a}{20} - \frac{v_a}{j5} - \frac{v_a - 140 - j30}{12 + j16} = 0$
 $\sum I_b = \frac{v_a - v_b}{12 + j16} - \frac{v_b}{-j10} + I_g + I_Z = 0 = \frac{v_a - 140 - j30}{12 + j16} - \frac{140 + j30}{-j10} + 30 + j20 - I_Z = 0$
 Solve $\sum I$ for $v_a = 40 + j30$ & $\sum I_b$ for $I_Z = -30 - j10$
 $Z = \frac{v_g - v_b}{I_Z} = \frac{(100 - j50) - (140 + j30)}{-30 - j10} = 2 + j2 \Omega$



6. 9.64 a) Find v_o if $i_g = 2 \cos(16 \cdot 10^5 t) \text{ A} \Rightarrow I_g = 2 \angle 0$

Source transformation

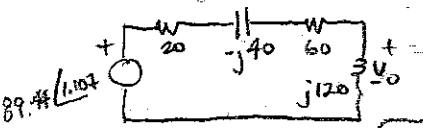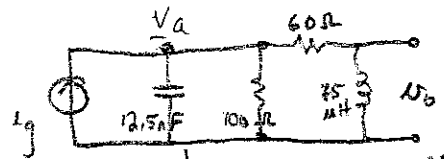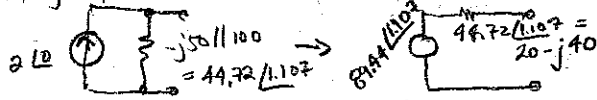

$$V_o = \frac{j120}{80 + j80} (89.44) / 1.107 = 94.87 \angle -18.43^\circ \text{ (degrees)}$$

$$Z_C = j(16 \times 10^5)(12.5 \times 10^{-9}) = -j50$$

$$Z_L = j(16 \times 10^5)(75 \times 10^{-6}) = j120$$

$$v_o = 94.87 \cos(16 \cdot 10^5 t - 18.43^\circ) \text{ V}$$

b.) Find time lag $T = \frac{2\pi}{\omega} = 1.25\pi \mu\text{s}$ so $\frac{18.43^\circ}{360^\circ} (1.25\pi) = 201.15 \mu\text{s}$ v_o lags i_g .