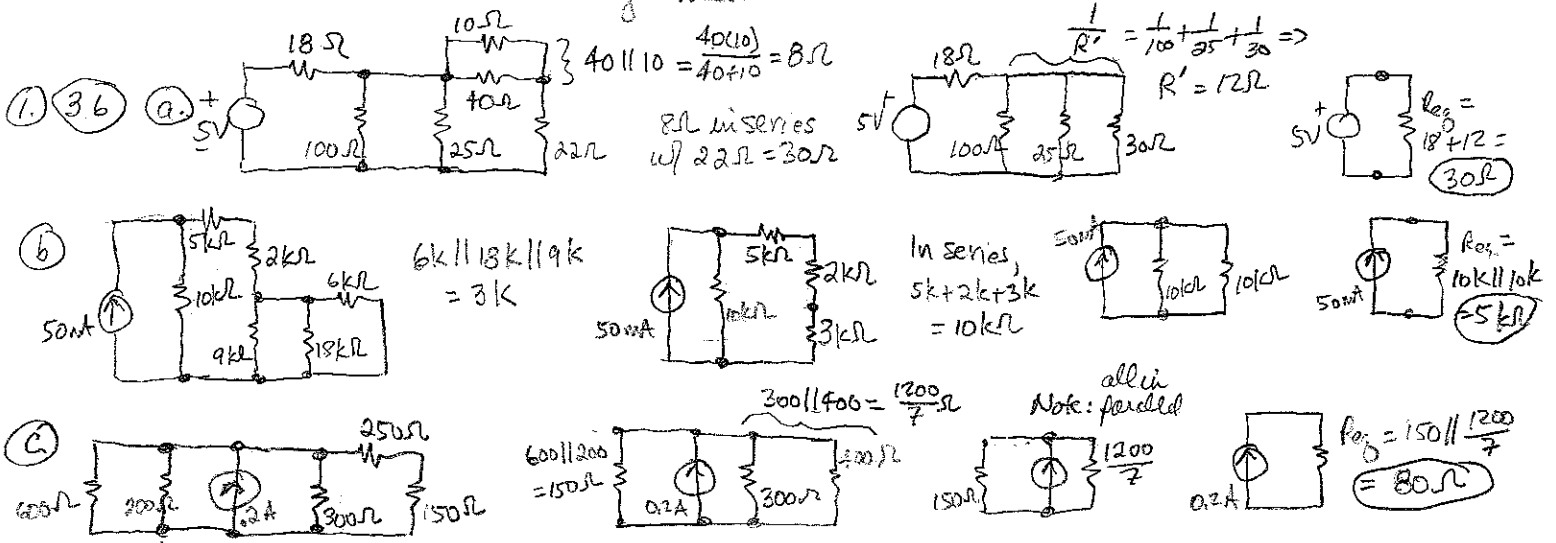


3.6, 4.14, 4.18a
4.36, 4.42a, 4.50, 4.54

Engineering II Electrical Circuit Analysis Assignment 2 Solutions

2005
LAM




② 4.14 a. Find V_1, V_2, V_3 using node voltage method.

$$\sum i = 0 = \frac{40 + V_2}{3} - \frac{V_1}{40} - \frac{V_1 - V_2}{2}$$

$$\sum i = 0 = \frac{V_1 - V_2}{2} - \frac{V_2 - V_3}{4} + 28$$
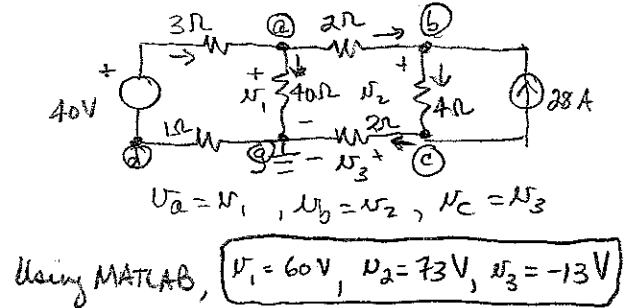
$$\sum i = 0 = \frac{V_2 - V_3}{4} - \frac{V_3}{2} - 28$$



① b. $P_{28A} = V_{28A} \cdot i_{28A} = (V_3 - V_2)(28) = (-86)(28) = -2408 W$ (power delivered since neg.)

③ 4.18a Find V_1, V_2, V_3 .


$$\sum i = 0 = 5i_0 - \frac{V_1}{20} - \frac{V_1 - V_2}{5}$$

$$\sum i = 0 = \frac{V_1 - V_2}{5} - \frac{V_2}{40} - \frac{V_2 - V_3}{10}$$

$$\sum i = 0 = \frac{V_2 - V_3}{10} - \frac{V_3 - 96}{4} - \frac{V_3 - 11.5i_0}{5}$$

Also read eq for i_0 :
 $i_0 = \frac{V_2}{40}$

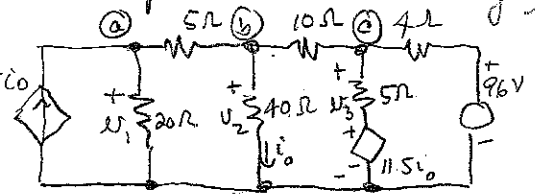Using MATLAB,
 $V_1 = 156V, V_2 = 120V, V_3 = 78V$




④ 4.36 Use mesh current to find v_0 .

$$\sum v = 0 = 10 - 2i_1 - 16(i_1 - i_2)$$

$$\sum v = 0 = 16(i_2 - i_1) + 12i_2 + 4i_2$$

$$\sum v = 0 = 4 - 5i_1 - 3i_2$$

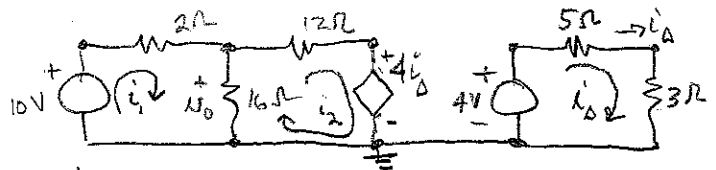Solve using MATLAB
 $\Rightarrow i_1 = 1A, i_2 = 0.5A, i_\Delta = 0.5A$



so $v_0 = 16(i_1 - i_2) = 8V$


① b. Find power delivered by dependent source. $P = (4i_\Delta)(i_2) = 2(\frac{1}{2}) = 1W$ absorbed (or -1W delivered.)

5) 4.42 @ Use mesh currents to find which sources are delivering power.

$$\sum W = 0 = 75 + 6i_1 + 12(i_1 - i_2) - 7i_\Delta$$

$$\sum_2 W = 0 = 7i_\Delta + 12(i_2 - i_1) + 15i_2 + 60(i_2 - i_3)$$

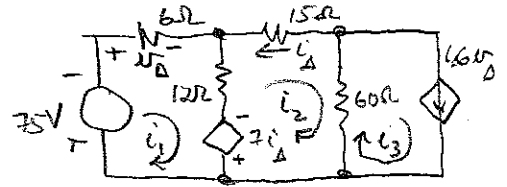Loop 3: $i_3 = 1.6i_\Delta = 1.6(6i_1) = 9.6i_1$; Dependent Source: $i_\Delta = -i_2$; $i_D = -29.4A$
 solve using MATLAB $\Rightarrow i_1 = 4A$, $i_2 = 29.4A$, $i_3 = 38.4A \Rightarrow v_\Delta = 6i_1 = 24V$
 $P_{75V} = 75(4) = 300W$, $P_{vccs} = (-540)(1.6)(24) = -20,736W$,
 $P_{ccs} = -7(-29.4)(4 - 29.4) = -5227W$




6) 4.50 Want power delivered by 4A source $\Rightarrow 0$

For no power from 4A source, need $v_{ab} = 0 \Rightarrow I_2 = -4A$

Then $\sum v = 0 = 240 - 12I_1 - 20(I_1 - I_2)$ (where $I_2 = -4$) $\Rightarrow I_1 = 5A$

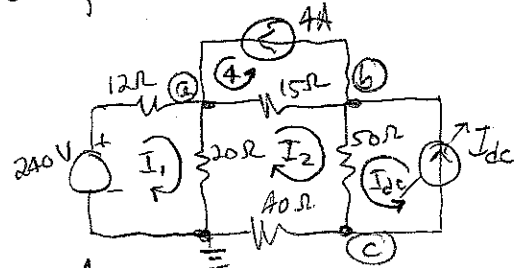And $\sum_2 v = 0 = 50(I_2 + I_{dc}) + 40I_2 + 20(I_2 - I_1) = 0$ (sub in I_1, I_2) $\Rightarrow I_{dc} = 10.8A$



7) 4.54 Use node voltage method since dependent sources require in terms of v's.
 (Consider ab & cd as supernodes.)

$$\frac{v_a}{100} + \frac{v_b}{250} - 0.2 + 0.003(v_\Delta = v_c) = 0$$

$$\text{where } v_b - v_a = 20$$

$$\frac{v_c}{500} + \frac{v_d}{200} - 0.003v_c + 0.2 = 0$$

$$v_a - v_c = 0.4v_a = 0.4v_b$$

$$\therefore v_b = 44V ; i_o = 0.2 - \frac{44}{250} = 0.024A$$

$$\text{a } P_{20V} = 20i_o = 480mW \text{ absorbed}$$

