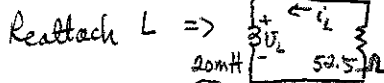



1. 7.11 a. Find $i_L(t)$ for $t > 0$. Find Thevenin equiv. of RHS using V_{test}, I_{test} .

$$V_{test} - 30i_{\Delta} - 90i_{\Delta} = 0$$

$$90i_{\Delta} = 70(i_{test} - i_{\Delta})$$



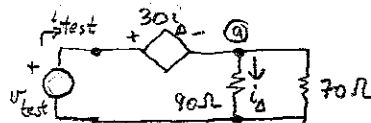
$$V_{test} = 120i_{\Delta} = 120 \left(\frac{70}{160} \right) i_{test}$$



$$R_T = \frac{V_{test}}{I_{test}} = 52.5 \Omega$$
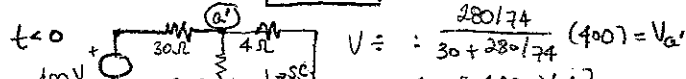
$$\text{Reattach } L \Rightarrow \frac{dL}{dt} + \frac{R}{L} i_L = 0 \Rightarrow s + \frac{52.5}{20 \times 10^{-3}} = 0 \Rightarrow s = -2625 \text{ so } i_L(t) = Ae^{-2625t}$$



$$V = \frac{280/74}{30 + 280/74} (400) = V_{oc}$$

$$I = \frac{70}{74} \left[\frac{400 - V_{oc}}{30} \right] = i_L(0^-) = 11.2 \text{ A}$$


$$i_L(t) = 11.2 e^{-2625t} \text{ A ; } t \geq 0$$

$$b. v_L(t) = L \frac{di_L}{dt} = -588 e^{-2625t} \text{ V ; } t \geq 0^+$$

$$c. v_L = 120i_{\Delta} \Rightarrow i_{\Delta} = -4.9 e^{-2625t} \text{ A ; } t \geq 0$$

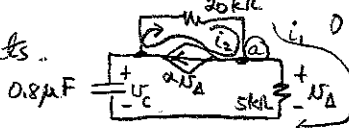2. 7.26 a. Find α for $\tau = 40 \text{ ms}$. Use loop currents.

$$\alpha = 2.5 \times 10^{-4} \text{ A/V}$$



$$i_1 = \frac{1}{s} \int i_1 dt + 20k(i_1 - 2i_2) + 5ki_1$$


$$\text{where } V_{\Delta} = 5ki_1 \Rightarrow \frac{1}{s(0.8\mu)} + (25k - 5k(20k)\alpha) = 0$$

b. Find V_{Δ} . For $t > 0, V_{\Delta} = -5(3.6) = -18 \text{ V} \Rightarrow$ for $t > 0, V_{\Delta}(t) = -18e^{-t/0.04} \text{ V ; } t \geq 0$

$$\sum i = 0 = \frac{V_{\Delta}}{5k} + \frac{V_{\Delta} - V_{\Delta}}{20k} + 25(10^{-4})V_{\Delta} = 0 \Rightarrow V_{\Delta} = -V_{\Delta}/10 = -1.8 e^{-t/0.04} \text{ V ; } t \geq 0^+$$

3. 7.48 a. Find $v_o(t)$. For $t < 0, v_o = 0$. For $t > 0$

$$v_o = v_{oh} + v_{op} = Ae^{-t/RC} + v_{op}; v_{op} = 5(60 || 15) = 60 \text{ V}$$

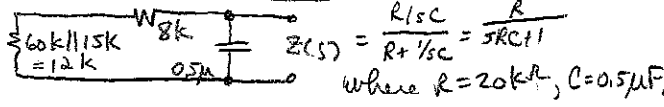

$$\therefore v_o = 60(1 - e^{-100t}) \text{ V ; } t \geq 0$$

$$i_o = \frac{v_o + 8k i_c}{60k} = 1 - 0.6 e^{-100t} \text{ mA ; } t \geq 0^+$$


b. Find $i_o(t)$. Use $i_c = C dv_o/dt = 3e^{-100t}$

c. Find $i_1(t) = i_o(t) + i_c(t) = 1 + 2.4e^{-100t} \text{ mA ; } t \geq 0^+$

$$d. i_2(t) = \frac{v_o + 8k i_c}{15k} = 4 - 2.4e^{-100t} \text{ mA}$$

e. Find $i_1(0^+) = 1 + 2.4 = 3.4 \text{ mA}$

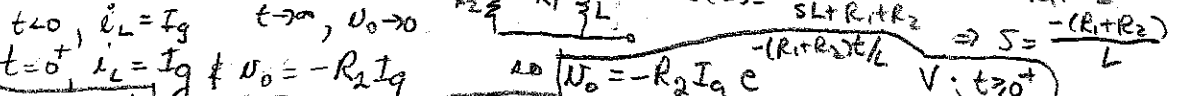3. 7.36 a. Find $v_o(t)$. $t < 0, i_L = I_g$ $t \rightarrow \infty, v_o \rightarrow 0$



$$t = 0^+, i_L = I_g \neq v_o = -R_2 I_g$$

$$\text{so } v_o = -R_2 I_g e^{-(R_1+R_2)t/L} \text{ V ; } t \geq 0^+$$

b. $v_o = -150 e^{-1250t} \text{ V ; } t \geq 0^+$

c. $\uparrow R_2 \Rightarrow$ Amplitude of $v_o \rightarrow \infty$; duration of $v_o \rightarrow \infty$

d. $v_{sw} = R_2 i_L$; $i_L = Be^{-(R_1+R_2)t/L}$ where $i_L(0) = I_g$; $i_{LP} = \frac{R_2}{R_1+R_2} I_g \Rightarrow I_g = B + \frac{R_2}{R_1+R_2} I_g$

$$\text{or } i_L = \frac{R_2 I_g}{R_1+R_2} e^{-(R_1+R_2)t/L} + \frac{R_2 I_g}{R_1+R_2} \Rightarrow v_{sw} = \frac{1}{4} \frac{R_2}{R_2} I_g \left[R_1 + R_2 e^{-(R_1+R_2)t/L} \right] \text{ V ; } t \geq 0^+$$

e. Same as for v_o .


3. 7.55 Find $v_o(t)$. For $t < 0, v_o = -3(15) = -45 \text{ V}$. For $t > 0$, find Thevenin equiv. of RHS w/o C using V_{test}, I_{test} .



$$V_{test} = -20(10^3)i_{\Delta} + 8(10^3)i_{test}; i_{\Delta} = \frac{10}{50} i_{test}$$

$$\Rightarrow v_{test} = 4(10^3)i_{test} \Rightarrow R_T = 4k\Omega$$
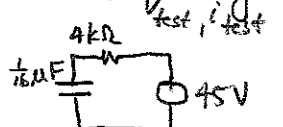
$$V_a = \frac{10}{50}(25) = 15 \text{ V}; V_T = V_a - (20(10^3)) \left(\frac{75}{50} \right) = 45 \text{ V}$$



$$\text{so } v_o(t) = Ae^{-t/RC} + v_{op}; v_{op} = 45 \text{ V (C} \rightarrow \text{a.c.)}; v_o(0) = -45 = A + 45 \text{ or } A = -90$$

$$\therefore v_o(t) = 45 - 90 e^{-4000t} \text{ V ; } t \geq 0$$

7.89 $v_- = v_+ = \frac{80}{80+20}(-45) = -36 \text{ V}$ $\sum i = \frac{14 - (-36)}{80k} + 25(10^{-6}) \frac{dv_o}{dt} (v_o - (-36)) \Rightarrow \frac{dv_o}{dt} = \frac{-50}{80k(2.5 \times 10^{-6})}$

$$\therefore v_o(t) = \int_{-\infty}^t \frac{dv_o}{dt} dt + \int_0^t \frac{dv_o}{dt} dt = v_o(0) - 850t; v_o(0) = -36 + 56 = 20 \text{ V} \therefore v_o(t) = 20 - 850t \text{ V}$$

$$v_o(t) = 0 \text{ @ } t = \frac{20}{850} = 0.0235 \text{ s}$$