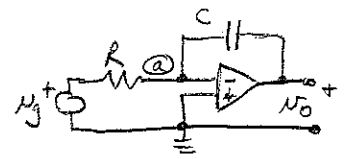


1. (7.96) Assume $v_c(0) = 0$.
 $C = 800 \text{ pF}$, $R = 1 \text{ k}\Omega$

$$v_g(t) = \begin{cases} \frac{2}{10^{-6}} t = 2(10^6) t & 0 \leq t \leq 1 \mu\text{s} \\ -2(10^6) t + 4 & 1 \leq t \leq 3 \mu\text{s} \\ 2(10^6) t - 8 & 3 \leq t \leq 4 \mu\text{s} \end{cases}$$




$$\sum i = 0 = \frac{v_g - v_o}{R} + C \frac{d}{dt}(v_o - 0) \Rightarrow \frac{dv_o}{dt} = -\frac{1}{RC} v_g \Rightarrow v_o = -\frac{1}{RC} \int_{-\infty}^t v_g(t) dt$$

Note: $\int_{-\infty}^t = \int_{-\infty}^0 + \int_0^t = \int_0^t$

$$v_o = 1.25(10^6) \left\{ \begin{aligned} & \left[-2(10^6) \frac{t^2}{2} \right]_0^t = -10^6 t^2 \quad (= -10^{-6} \text{ @ } t = 1 \mu\text{s}) \\ & - \left[2(10^6) \frac{t^2}{2} + 4t \right]_{1 \mu\text{s}}^t = 10^6 t^2 - 4t - [1(10^6)(10^{-12}) - 4(10^{-6})] - 10^{-6} = 10^6 t^2 - 4t + 2(10^{-6}) \quad (= -10^{-6} \text{ @ } 3 \mu\text{s}) \\ & - \left[2(10^6) \frac{t^2}{2} - 8t \right]_{3 \mu\text{s}}^t = -1(10^6) t^2 + 8t - [-10^6(9)(10^{-12}) + 8(3 \times 10^{-6})] - 10^{-6} = -10^6 t^2 + 8t - 16(10^{-6}) \end{aligned} \right.$$


where we used $\int_{-\infty}^t = \int_{-\infty}^0 + \int_0^{1 \mu\text{s}} + \int_{1 \mu\text{s}}^t$ for $1 \leq t \leq 3 \mu\text{s}$
 $\int_{-\infty}^t = \int_{-\infty}^0 + \int_0^{1 \mu\text{s}} + \int_{1 \mu\text{s}}^{3 \mu\text{s}} + \int_{3 \mu\text{s}}^t$ for $3 \leq t \leq 4 \mu\text{s}$
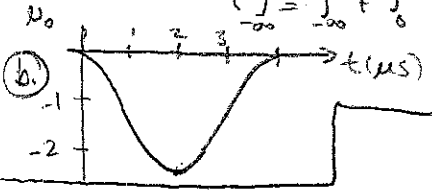
$$v(t) = \begin{cases} -1.25(10^{12}) t^2 \text{ V} & 0 \leq t \leq 1 \mu\text{s} \\ 1.25(10^{12}) t^2 - 5(10^6) t + 2.5 \text{ V} & 1 \leq t \leq 3 \mu\text{s} \\ -1.25(10^{12}) t^2 + 10(10^6) t - 20 \text{ V} & 3 \leq t \leq 4 \mu\text{s} \end{cases}$$



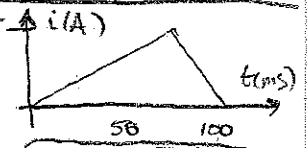c. Yes, this repeats since $v_o = 0$ when the input begins to repeat.

$$i(t) = \begin{cases} 200t & 0 \leq t \leq 75 \text{ ms} \\ 60 - 600t & 75 \leq t \leq 100 \text{ ms} \end{cases} \quad I_{\text{RMS}} = \sqrt{\frac{1}{T} \int_0^T i^2(t) dt}$$




2. (10.7)

Find RMS value.
 $I_{\text{RMS}} = \frac{1}{100 \text{ ms}} \left\{ \int_0^{75 \text{ ms}} (200t)^2 dt + \int_{75 \text{ ms}}^{100 \text{ ms}} (60 - 600t)^2 dt \right\} = 10(5.625) + 10(1.875) = 75$

$I_{\text{RMS}} = \sqrt{75} \text{ A}$

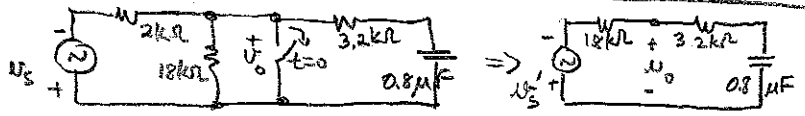3. For a sinusoidal source, $\omega = 1000$, find $v_o(t)$.

$v_s = 40 \cos(1000t)$; by source transformation, $v_s' = 36 \cos(1000t)$



For $t < 0$, switch closed, $v_o = 0$. For $t > 0$, $v_o = v_{oh} + v_{op}$. Use $v_c(0^-) = v_c(0^+) = 0$.

Homogeneous: $R_1 \parallel \frac{1}{sC} \parallel R$ $Z(s) = R_1 \parallel (R + \frac{1}{sC}) = R_1 \parallel \frac{sRC + 1}{sC} = \frac{sRC + 1}{sRC + sRC + 1}$ Use poles for $v_{oh} \Rightarrow s = \frac{-1}{(R_1 + R)C}$

Particular: use voltage divider with impedances/phasors $v_{op} = \frac{3.2 \text{ k}\Omega + \frac{1}{j(0.8 \times 10^{-3})}}{1.8 \text{ k}\Omega + 3.2 \text{ k}\Omega + \frac{1}{j(0.8 \times 10^{-3})}} v_s' = \frac{3.2 - j1.2}{5 - j1.2} v_s' = \frac{3.418 \angle -20.56^\circ}{5.142 \angle -13.5^\circ} (-23) = -15.3 \angle -7.06^\circ$


$v_o = A e^{-250t} + 15.3 \cos(1000t - 172.8^\circ)$; $v_o(0) = \frac{3.2}{3.2 + 1.8} (-36) = -23 = A + 15.3 \Rightarrow A = -38.3$

$v_o(t) = -38.3 e^{-250t} + 15.3 \cos(1000t - 172.8^\circ) \text{ V}$

Note: other equivalent forms of this solution exist.

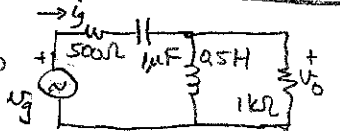4. Let $v_g = 20 \cos 2000t$. Insert S that closes @ $t = 0$. Assume $v_c(0^-) = i_L(0^-) = 0$

From previous week, $v_{op} = 14.14 \cos(\omega t + \pi/4)$. Find v_{oh} using $Z(s)$.



$Y(s) = \frac{1}{R_1} + \frac{1}{sL} + \frac{1}{R_2 + 1/sC} = \frac{s^2(CR_2R_1)LC + s(RR_1C + L) + R_1}{sR_1L(sRC + 1)}$; use Zeros of Y for v_{oh}
 $s^2 + s \frac{RR_1C + L}{(R_1 + R_2)LC} + \frac{R_1}{(R_1 + R_2)LC} = 0$; solve for s using above values.



Finished (Cs in class).