

# E12 ASSIGNMENT 6 SOLUTIONS

## 5.13

We do not include the gravitational force  $Mg$  in the free-body diagram for the mass, because displacements are measured from the static equilibrium condition caused by gravity. Note that the free-body diagram for the lever is labeled with torques. From (5), we obtain

$$J_A = \frac{M}{3L} \left[ \left(\frac{L}{4}\right)^3 + \left(\frac{3L}{4}\right)^3 \right] = \frac{7ML^2}{48}$$

In drawing the diagrams, we used  $x_2 = (L/4)\theta$ ,  $x_3 = (3L/4)\theta$ , and  $v_3 = (3L/4)\omega$ . Summing the forces on the mass and summing the torques about the lever's pivot point, we have



$$\begin{aligned} M\dot{v}_1 + B_1v_1 + (K_1 + K_2)x_1 - \frac{LK_2\theta}{4} &= 0 \\ \frac{7ML^2}{48}\dot{\omega} + \frac{9L^2B_2}{16}\omega + \frac{L^2K_2}{16}\theta - \frac{LK_2}{4}x_1 + \frac{3L}{4}f_a(t) &= 0 \end{aligned}$$

We select  $x_1$ ,  $v_1$ ,  $\theta$ , and  $\omega$  as the state variables and write

$$\begin{aligned} \dot{x} &= v \\ \dot{v} &= \frac{1}{M} \left[ -(K_1 + K_2)x_1 - B_1v_1 + \frac{LK_2\theta}{4} \right] \\ \dot{\theta} &= \omega \\ \dot{\omega} &= \frac{3}{7ML} [4K_2x_1 - LK_2\theta - 9LB_2\omega - 12f_a(t)] \end{aligned}$$

The output equation is
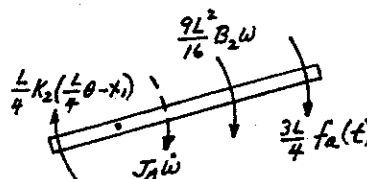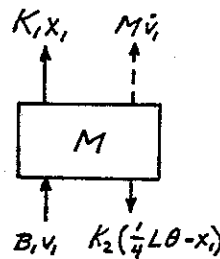
$$f_{K_2} = -K_2x + \frac{LK_2}{4}\theta$$



## 6.9

Let  $e_A$  denote the node voltage at the top of the inductor, and  $i_L$  the current down through the inductor. Applying Kirchhoff's current law to nodes  $A$  and  $O$  gives

$$-i_i(t) + i_L(0) + \frac{1}{8} \int_0^t e_A d\lambda + \frac{1}{4}(e_A - e_o) = 0 \quad (A)$$

$$\frac{1}{4}(e_o - e_A) + \frac{1}{2}\dot{e}_o + \frac{1}{4}e_o = 0 \quad (B)$$

Differentiating (A) and simplifying both equations, we obtain

$$2\dot{e}_A + e_A - 2\dot{e}_o = 8\frac{di_i}{dt} \quad (C)$$

$$e_A = 2\dot{e}_o + 2e_o \quad (D)$$


Substituting (D) into (C), we get

$$\dot{e}_o + \dot{e}_o + \frac{1}{2}e_o = 2\frac{di_i}{dt}$$
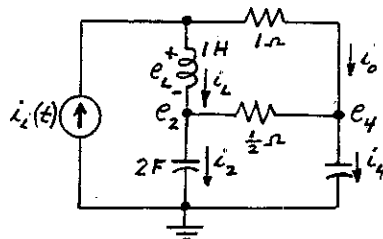
## 6.25

We choose  $e_2$ ,  $e_4$ , and  $i_L$  as the state variables. The output equation is  $i_o = i_i(t) - i_L$ . Summing the currents leaving node 2, the currents leaving node 4, and the voltages around a closed path that contains the inductor and the capacitors, we have

$$\begin{aligned} i_2 + 2(e_2 - e_4) - i_L &= 0 \\ i_4 + 2(e_4 - e_2) - [i_i(t) - i_L] &= 0 \\ e_2 + e_L - e_4 - [i_i(t) - i_L] &= 0 \end{aligned}$$



We solve these equations for  $i_2$ ,  $i_4$ , and  $e_2$  and then use the element laws  $\dot{e}_2 = 0.5i_2$ ,  $\dot{e}_4 = 0.25i_4$ , and  $di_L/dt = e_L$  in order to get the state-variable equations.

$$\begin{aligned} \dot{e}_2 &= -e_2 + e_4 + \frac{1}{2}i_L \\ \dot{e}_4 &= \frac{1}{2}e_2 - \frac{1}{2}e_4 - \frac{1}{4}i_L + \frac{1}{4}i_i(t) \\ \frac{di_L}{dt} &= -e_2 + e_4 - i_L + i_i(t) \end{aligned}$$

### 6.30

(a) Because  $i_A + i_B = i_i(t)$ , we have only one state variable, which we initially choose to be  $i_A$ . By Kirchhoff's voltage law,

$$L_1 \frac{di_A}{dt} + R_1 i_A = L_2 \frac{di_B}{dt} + R_2 i_B$$

Replacing  $i_B$  by  $i_i(t) - i_A$  gives

$$(L_1 + L_2) \frac{di_A}{dt} + (R_1 + R_2) i_A = L_2 \frac{di_i}{dt} + R_2 i_i(t)$$

Defining the new state variable

$$x = (L_1 + L_2) i_A - L_2 i_i(t)$$

we get

$$\dot{x} = - \left( \frac{R_1 + R_2}{L_1 + L_2} \right) x + \left( \frac{R_2 L_1 - R_1 L_2}{L_1 + L_2} \right) i_i(t)$$

where

$$i_A = \frac{1}{L_1 + L_2} [x + L_2 i_i(t)]$$

(b) The output voltage  $e_o$  is given by

$$e_o = L_1 \frac{di_A}{dt} + R_1 i_A = \frac{1}{L_1 + L_2} \left[ L_1 \dot{x} + L_1 L_2 \frac{di_i}{dt} + R_1 x + R_1 L_2 i_i(t) \right]$$

Inserting the expression for  $\dot{x}$  and simplifying the result, we find that

$$e_o = \frac{1}{(L_1 + L_2)^2} \left[ (R_1 L_2 - R_2 L_1) x + L_1 L_2 (L_1 + L_2) \frac{di_i}{dt} + (R_2 L_1^2 + R_1 L_2^2) i_i(t) \right]$$

In this situation, we cannot avoid a derivative of the input on the right side of the output equation.

### 6.33

Let  $e_A$  and  $e_B$  denote the voltages at the inverting and noninverting terminals, respectively, of the op-amp. Summing the currents leaving node  $A$  gives

$$\frac{1}{R_1} e_A + \frac{1}{R_2} (e_A - e_o) + C(\dot{e}_A - \dot{e}_o) = 0 \quad (\text{A})$$

Because no current enters the input terminals of the op-amp, we use the voltage-divider rule to write

$$e_B = \frac{R_4}{R_3 + R_4} e_i(t) \quad (\text{B})$$

By the virtual-short concept,  $e_B = e_A$ . Using this fact, we substitute (B) into (A) to obtain

$$C \dot{e}_o + \frac{1}{R_2} e_o = \frac{R_4}{R_3 + R_4} \left[ C \dot{e}_i + \frac{R_1 + R_2}{R_1 R_2} e_i(t) \right]$$